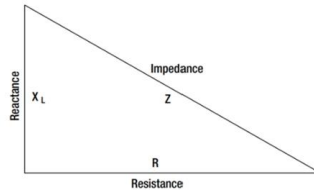


Resistive (R), Capacitive (C) and Inductive (L) circuits

Series AC Circuits

Impedance: may be illustrated by a right triangle.



$$Z^2 = R^2 + X_L^2$$

The square root of both sides of the equation gives:

$$Z = \sqrt{R^2 + X_L^2}$$

Resistance and reactance cannot be added directly, but they can be considered as two forces acting at right angles to each other

EX:

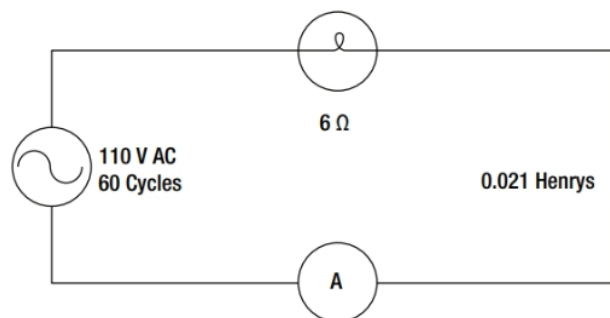


Figure 14-3. A circuit containing resistance and inductance.

$$X_L = 2 \pi \times f \times L$$

$$X_L = 6.28 \times 60 \times 0.021$$

$$X_L = 8 \text{ ohms inductive reactance}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{6^2 + 8^2}$$

$$Z = \sqrt{36 + 64}$$

$$Z = \sqrt{100}$$

$$Z = 10 \text{ ohms impedance}$$

The voltage drop across the resistance (E_R) is:

$$E^R = I \times R$$

$$E^R = 11 \times 6 = 66 \text{ volts}$$

The voltage drop across the inductance (E_{X_L}) is:

$$E_{X_L} = I \times X_L$$

$$E_{X_L} = 11 \times 8 = 88 \text{ volts}$$


Then the current flow,

$$I = \frac{E}{Z}$$

$$I = \frac{110}{10}$$

$$I = 11 \text{ amperes current}$$

Ex:

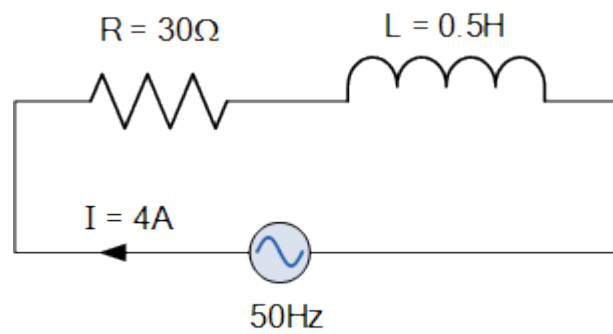

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.5 = 157\Omega$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{30^2 + 157^2}$$


$$Z = 159.8\Omega$$

$$V_S = IZ = 4 \times 159.8 = 640v$$

$$V_R = I.R = 4 \times 30 = 120v$$

$$V_L = I.X_L = 4 \times 157 = 628v$$
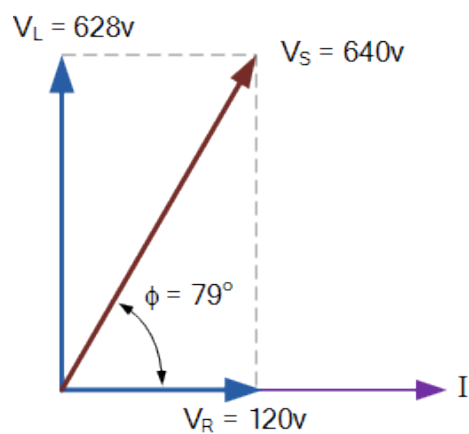
$$\tan^{-1}\phi = \frac{X_L}{R} = \frac{157}{30} = 79.2^\circ \quad \text{Phase angel}$$



Ex: Rc

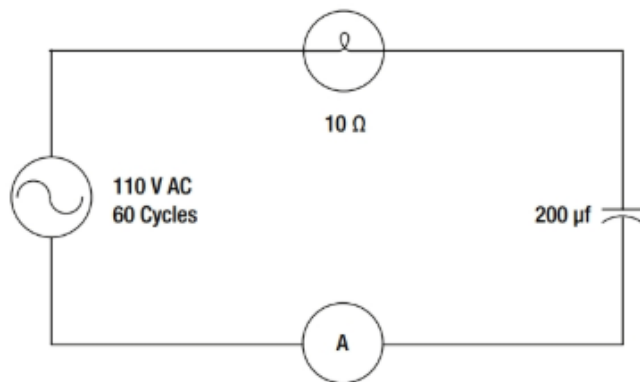


Figure 14-4. A circuit containing resistance and capacitance.

$$200 \mu\text{f} = \frac{200}{1\,000\,000} = 0.000\,200 \text{ farads}$$

$$X_C = \frac{1}{2 \pi f C}$$

$$X_C = \frac{1}{6.28 \times 60 \times 0.000\,200 \text{ farads}}$$

$$X_C = \frac{1}{0.075\,36}$$

$$X_C = 13 \text{ ohms capacitive reactance}$$

To find the impedance:

$$Z = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{10^2 + 13^2}$$

$$Z = \sqrt{100 + 169}$$

$$Z = \sqrt{269}$$

$$Z = 16.4 \text{ ohms capacitive reactance}$$


To find the current:

$$I = \frac{E}{Z}$$

$$I = \frac{110}{16.4}$$

$$I = 6.7 \text{ amperes}$$

Ex: RLC

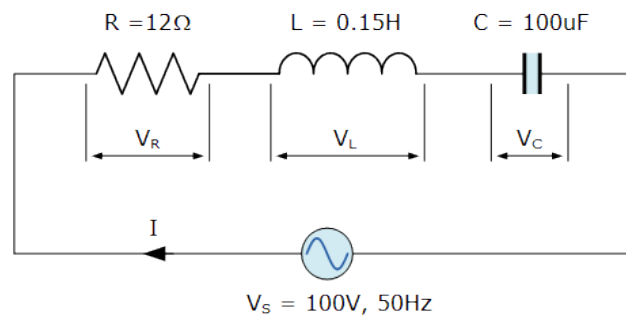

$$V_s = 100V, 50Hz$$

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.15 = 47.13\Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.83\Omega$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{12^2 + (47.13 - 31.83)^2}$$

$$Z = \sqrt{144 + 234} = 19.4\Omega$$

$$I = \frac{V_s}{Z} = \frac{100}{19.4} = 5.14\text{Amps}$$

Parallel AC Circuits

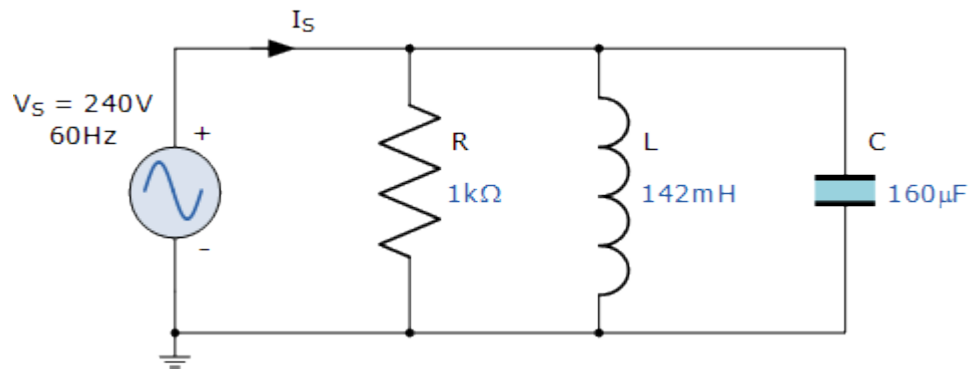

$$X_L = \omega L = 2\pi f L = 2\pi \cdot 60 \cdot 142 \times 10^{-3} = 53.54 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \cdot 60 \cdot 160 \times 10^{-6}} = 16.58 \Omega$$

$$I_L = \frac{V}{X_L} \quad I_C = \frac{V}{X_C}$$


$$I_L = \frac{240}{53.54} = 4.48A \quad I_C = \frac{240}{16.58} = 14.4A \quad I_R = \frac{240}{1000} = 0.24A$$

$$I = \sqrt{I_R^2 + (I_L - I_C)^2} \quad I = \sqrt{(0.24)^2 + (4.48 - 14.4)^2} = 9.9A$$

$$Z = \frac{V}{I} = \frac{240}{9.9} = 24.24 \Omega$$

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}} = \frac{1}{\sqrt{\left(\frac{1}{1000}\right)^2 + \left(\frac{1}{53.54} - \frac{1}{16.58}\right)^2}}$$

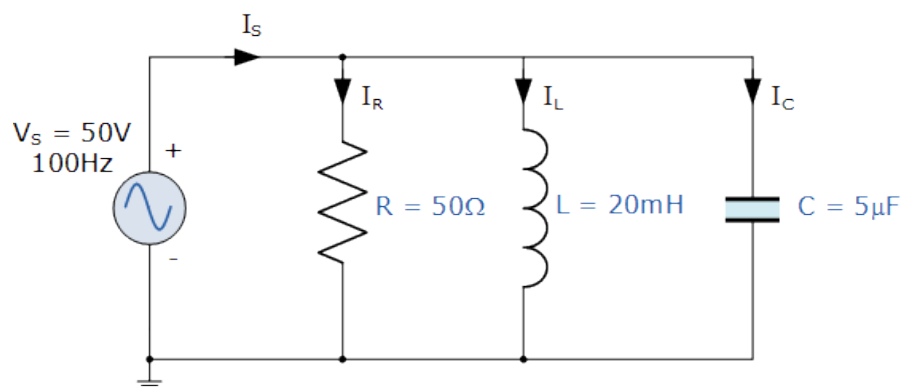
$$Z = \frac{1}{\sqrt{1.0 \times 10^{-6} + 1.734 \times 10^{-3}}} = \frac{1}{0.0417} = 24.0 \Omega$$





Series Resonance Circuit

Resonance occurs in a series circuit when the supply frequency causes the voltages across L and C to be equal and opposite in phase.

Inductive Reactance against Frequency

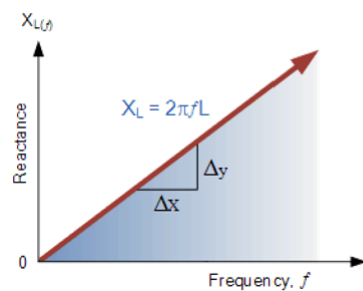

Capacitive Reactance against Frequency

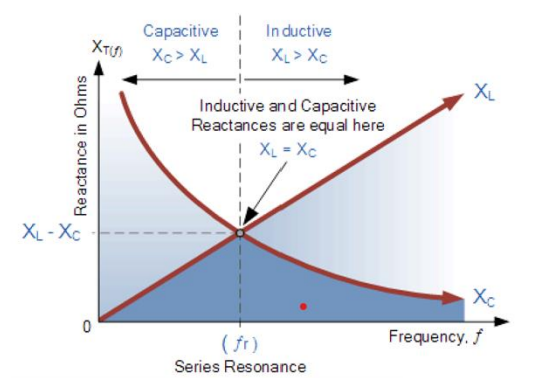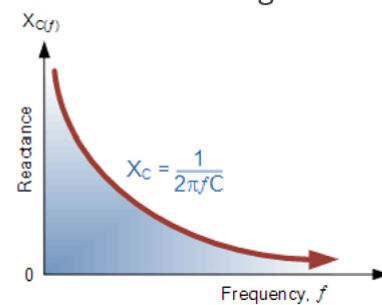

Resonance occurs in a series circuit when the supply frequency causes the voltages across L and C to be equal and opposite in phase. ■


$$X_L = X_C \Rightarrow 2\pi fL = \frac{1}{2\pi fC}$$

$$f^2 = \frac{1}{2\pi L \times 2\pi C} = \frac{1}{4\pi^2 LC}$$

$$f = \sqrt{\frac{1}{4\pi^2 LC}}$$

$$\therefore f_r = \frac{1}{2\pi\sqrt{LC}} \text{ (Hz)} \quad \text{or} \quad \omega_r = \frac{1}{\sqrt{LC}} \text{ (rads)}$$

Ex:

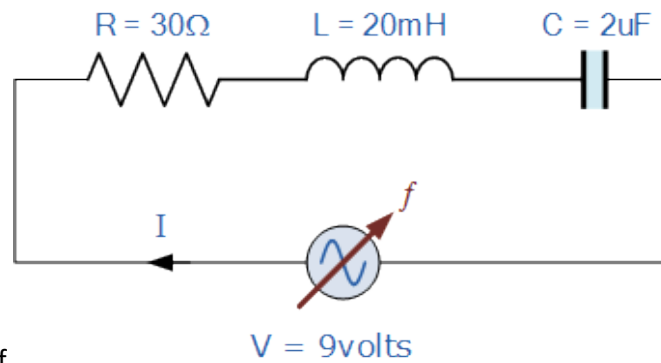

Resonant Frequency, f_r

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.02 \times 2 \times 10^{-6}}} = 796\text{Hz}$$

Circuit Current at Resonance, I_m

$$I = \frac{V}{R} = \frac{9}{30} = 0.3\text{A or } 300\text{mA}$$

Inductive Reactance at Resonance, X_L

$$X_L = 2\pi fL = 2\pi \times 796 \times 0.02 = 100\Omega$$

Voltages across the inductor and the capacitor, V_L , V_C

$$V_L = V_C$$

$$V_L = I \times X_L = 300\text{mA} \times 100\Omega$$

$$V_L = 30\text{volts}$$

I did not calculate the X_C because its resonance frequency.

Power in AC Circuits

true power: is the product of the volts and the amperes in the circuit.

True Power Defined

1, The power dissipated in the resistance of a circuit, or the power actually used in the circuit.

2, In an AC circuit, a voltmeter indicates the effective voltage and an ammeter indicates the effective current.

Apparent Power Defined

1, It is the product of effective voltage times the effective current, expressed in volt-amperes.

2, It must be multiplied by the power factor to obtain true power available.

Power in AC Circuits

the true power is less than the apparent power. When there is capacitance or inductance in the circuit, the current and voltage are not exactly in phase,

power factor

power factor: is The ratio of the true power to the apparent power and is usually expressed in percent.

$$\text{Power Factor (PF)} = \frac{100 \times \text{Watts (True Power)}}{\text{Volts} \times \text{Amperes (Apparent Power)}}$$

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$

*Measured in units of **Watts***

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

*Measured in units of **Volt-Amps-Reactive (VAR)***

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

*Measured in units of **Volt-Amps (VA)***

$$pr = \sqrt{pa^2 - pt^2}$$

Phase angle: formulas

$$\tan^{-1} \frac{X}{R} \quad \text{or} \quad \tan^{-1} \frac{VL - VC}{VR}$$

$$\cos^{-1} \frac{R}{Z} \quad \text{or} \quad \cos^{-1} \frac{VR}{VS}$$

$$\sin^{-1} \frac{X}{Z} \quad \text{or} \quad \sin^{-1} \frac{VL - VC}{VS}$$

